



Laboratório Digital I - PCS3635

Planejamento da Experiência 6:

Projeto Base do Jogo do Desafio da Memória

Marco Aurélio C. O. Prado - NUSP 11257605

Victor Hoefling Padula - NUSP 10770051

Turma 04 - Bancada A1

São Paulo - SP

23/02/2021

1) Objetivo

Os objetivos da aula consistem em aprender sobre:

- Projeto de circuitos usando descrição estrutural VHDL;
- Interface de circuitos digitais com elementos externos de entrada de dados;
- Documentação de projetos (planejamento e relatório);
- Uso de sinais periódicos como clock;

2) Elaboração do Circuito “circuito_exp6.vhd”

2.1) Descrição do funcionamento do circuito

O circuito é composto de uma unidade de controle e um fluxo de dados com 2 contadores, 2 comparadores, 1 memória, 1 registrador, conversores para 7 segmentos e 1 detector de jogadas. O circuito basicamente segue uma lógica de ter um contador limitando a contagem de outro contador que incrementa os endereços da memória. Isso é feito usando um comparador que verifica se o endereço é menor que o limite. Quando o endereço é igual ao limite, ele incrementa 1 ao contador de limite e repete a lógica do circuito.

2.2) Descrição VHDL do circuito “circuito_exp6.vhd”

O código da unidade de controle segue a seguinte lógica:

```
library ieee;
use ieee.std_logic_1164.all;

entity unidade_controle is
    port (
        clock:      in  std_logic;
        reset:      in  std_logic;
        iniciar:    in  std_logic;
        fimC:       in  std_logic;
        fimL:       in  std_logic;
        jogada:     in std_logic;
        enderecoIgualLimite: in std_logic;
        zera:       out std_logic;
        conta_end:  out std_logic;
        conta_lim:  out std_logic;
        zera_lim:   out std_logic;
        pronto:    out std_logic;
        db_estado:  out std_logic_vector(3 downto 0);
```

```

        acertou: out std_logic;
        errou: out std_logic;
        registra: out std_logic;
        igual: in std_logic
    );
end entity;

architecture fsm of unidade_controle is
    type t_estado is (A, B, C, D, E, F, M,J,L,R);
    signal Eatual, Eprox: t_estado;
begin
    -- memoria de estado
    process (clock,reset)
    begin
        if reset='1' then
            Eatual <= A;
        elsif clock'event and clock = '1' then
            Eatual <= Eprox;
        end if;
    end process;

    -- logica de proximo estado
    Eprox <=
        A when Eatual=A and iniciar='0' else
        B when Eatual=A and iniciar='1' else
        J when Eatual=B else
        J when Eatual=J and jogada='0' else
        M when Eatual=J and jogada='1' else
        C when Eatual=M else
        D when Eatual=C and enderecoIgualLimite='0' and igual='1' else
        F when Eatual=C and igual='0' else
        L when Eatual=C and enderecoIgualLimite='1' and igual='1'
    else
        J when Eatual=D else
        J when Eatual=L else
        E when Eatual=C and FimC='1' and igual='1' else
        B when Eatual=E and iniciar='1' else
        E when Eatual=E and iniciar='0' else
        B when Eatual=F and iniciar='1' else
        F when Eatual=F and iniciar='0' else

```

```

A;

-- logica de saída (maquina de Moore)
with Eatual select
    registra <= '0' when A | B | C | D | E | F | J,
               '1' when M,
               '0' when others;
with Eatual select

    zera <=    '0' when A | C | D | E | F | M | J,
               '1' when B | L,
               '0' when others;

with Eatual select
    conta_end <= '0' when A | B | C | E | F | M | J,
                 '1' when D,
                 '0' when others;

with Eatual select
    conta_lim <= '0' when A | B | C | E | F | M | J | D,
                 '1' when L,
                 '0' when others;

with Eatual select
    zera_lim <= '0' when A | C | E | F | M | J | D | L,
                '1' when B,
                '0' when others;

with Eatual select
    pronto <= '0' when A | B | C | D | M | J,
              '1' when E | F ,
              '0' when others;

with Eatual select
    acertou <='0' when A | B | C | D | F | M | J,
              '1' when E,
              '0' when others;

with Eatual select
    erro <= '0' when A | B | C | D | E | M | J,

```



```

        '1' when F,
        '0' when others;

-- saida de depuracao (db_estado)
with Eatual select
    db_estado <= "0000" when A,      -- 0
        "1011" when B,      -- B
        "1100" when C,      -- C
        "1101" when D,      -- D
        "1110" when E,      -- E
        "0111" when M, -- M
        "1000" when J,  -- J
        "1001" when L,
        "1111" when F,      -- F
        "0001" when others;  -- 1
end fsm;

```

Diagrama:

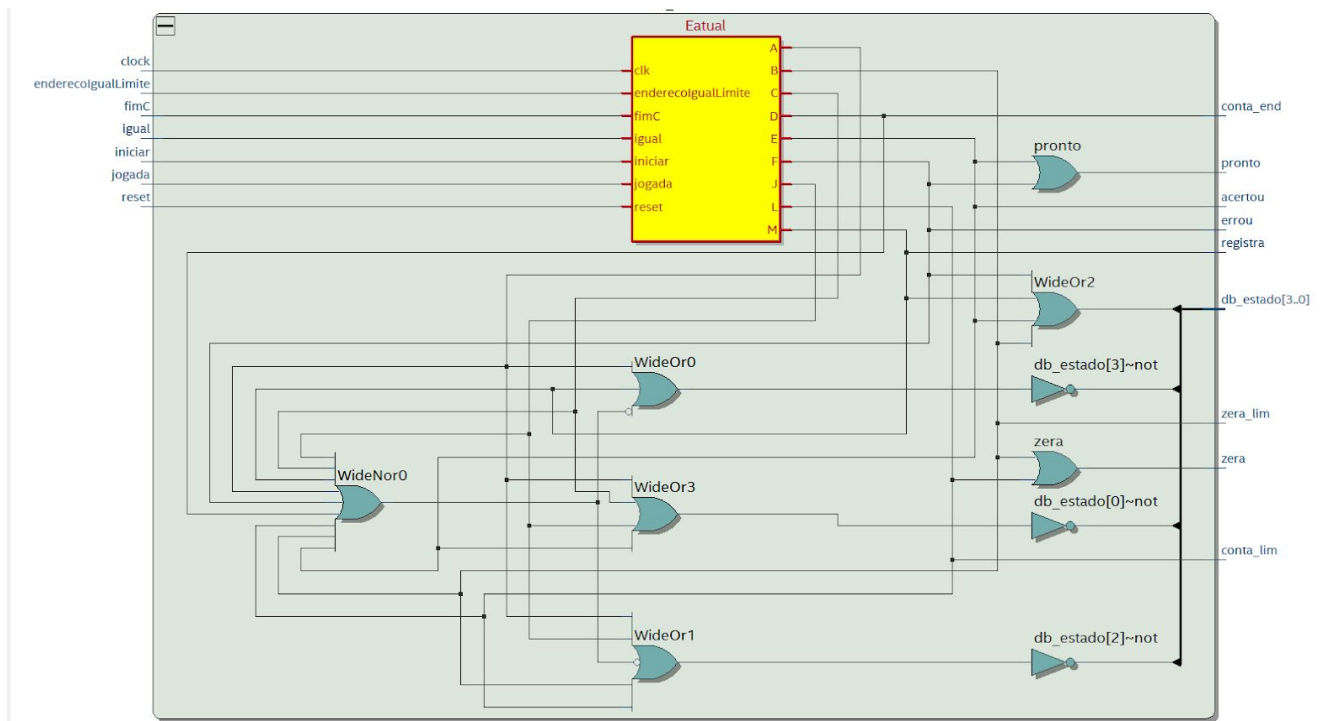 

O fluxo de dados segue a seguinte lógica:

```
library ieee;
use ieee.std_logic_1164.all;

entity fluxo_dados is
    port (
        clock : in std_logic;
        zeraE : in std_logic;
        limpaR: in std_logic;
```

```

    registraR: in std_logic;
    zeraL: in std_logic;
    contaL: in std_logic;
    contaE : in std_logic;
    escreve: in std_logic;
    botoes : in std_logic_vector (3 downto 0);
    fimE: out std_logic;
    fimL: out std_logic;
    db_tem_jogada: out std_logic;
    db_contagem : out std_logic_vector (3 downto 0);
    db_memoria: out std_logic_vector(3 downto 0);
    db_limite: out std_logic_vector (3 downto 0);
    jogada_feita: out std_logic;
    db_jogada: out std_logic_vector (3 downto 0);
    chavesIgualMemoria: out std_logic;
    enderecoMenorOuIgualLimite: out std_logic;
    enderecoIgualLimite: out std_logic
);
end entity fluxo_dados;

```

architecture estrutural of fluxo_dados is

```

    component contador_163 is
        port (
            clock : in  std_logic;
            clr   : in  std_logic;
            ld    : in  std_logic;
            ent   : in  std_logic;
            enp   : in  std_logic;
            D     : in  std_logic_vector (3 downto 0);
            Q     : out std_logic_vector (3 downto 0);
            rco   : out std_logic
        );
    end component;

```

```

    component comparador_85 is
        port (  -- entradas
            i_A3 : in  std_logic;

```

```

i_B3    : in  std_logic;
i_A2    : in  std_logic;
i_B2    : in  std_logic;
i_A1    : in  std_logic;
i_B1    : in  std_logic;
i_A0    : in  std_logic;
i_B0    : in  std_logic;
i_AGTB  : in  std_logic;
i_ALTB  : in  std_logic;
i_AEQB  : in  std_logic;
-- saidas
o_AGTB  : out std_logic;
o_ALTB  : out std_logic;
o_AEQB  : out std_logic
    );
end component;

component ram_16x4 is
    port(
        clk          : in  std_logic;
        endereco: in std_logic_vector(3 downto 0);
        dado_entrada: in std_logic_vector(3 downto 0);
        we: in std_logic;
        ce: in std_logic;
        dado_saida: out std_logic_vector(3 downto 0)
    );
end component;

component registrador_4bits is
    port (
        clock: in  std_logic;
        clear: in  std_logic;
        enable: in  std_logic;
        D:      in  std_logic_vector(3 downto 0);
        Q:      out std_logic_vector(3 downto 0)
    );

```



```

end component;

component edge_detector is
  port (
    clock   : in  std_logic;
    reset   : in  std_logic;
    sinal   : in  std_logic;
    pulso    : out std_logic);
end component;

-- Component instantiation
great, zeraE_baixo, igual_out, menor, great_o, menor_o, enable_cin, rco_outC, or_JGD, zeraL_baixo, rco_outL, fim_L: std_logic;
signal enderecoMenorqueLimite, IgualLimite: std_logic;
signal s_jogada: std_logic_vector (3 downto 0);
signal contador_out, s_dado, s_endereco, s_lim: std_logic_vector (3 downto 0);
begin

  zeraE_baixo <= not zeraE;
  Contend: contador_163 port map (
    clock => clock,
    clr   => zeraE_baixo,
    ld    => '1',
    ent   => '1',
    enp   => enable_Cin,
    D     => "0000",
    Q     => s_endereco,
    rco   => rco_outC
  );
  fimE <= rco_outC;
  ZeraL_baixo <= not ZeraL;
  Contlim: contador_163 port map (
    clock => clock,
    clr   => ZeraL_baixo,
    ld    => '1',
    ent   => '1',
    enp   => contaL,
    D     => "0000",

```

```

        Q      => s_lim,
        rco    => rco_outL
    );
    fimL<=rco_outL;
    db_limite<=s_lim;
    enable_Cin<=contaE;
    db_contagem<=s_endereco;

    complim: comparador_85 port map (
        i_A3  =>s_endereco(3),
        i_B3   => s_lim(3),
        i_A2   =>s_endereco(2),
        i_B2   => s_lim(2),
        i_A1   =>s_endereco(1),
        i_B1   => s_lim(1),
        i_A0   =>s_endereco(0),
        i_B0   => s_lim(0),
        i_AGTB =>'0',
        i_ALTB => '0',
        i_AEQB => '1',
        -- saidas
        o_ALTB =>enderecoMenorQueLimite,
        o_AEQB =>IgualLimite
    );
    enderecoIgualLimite<=IgualLimite;
    enderecoMenorOuIgualLimite<= enderecoMenorQueLimite or
IgualLimite;

    compJog: comparador_85 port map (
        i_A3  =>s_dado(3),
        i_B3   => botoes(3),
        i_A2   =>s_dado(2),
        i_B2   => botoes(2),
        i_A1   =>s_dado(1),
        i_B1   => botoes(1),
        i_A0   =>s_dado(0),
        i_B0   => botoes(0),
        i_AGTB =>'0',
        i_ALTB => '0',
        i_AEQB => '1',

```

```


        -- saidas
        o_AGTB => great,
        o_ALTB => menor,
        o_AEQB => igual_out
    );

    memoria: ram_16x4 port map(
        clk=> clock,
        endereco => s_endereco,
        dado_entrada => s_jogada,
        we => escreve,
        ce => '0',
        dado_saida => s_dado
    );
    db_memoria<=s_dado;
    chavesIgualMemoria<=igual_out;

    RegBotoes: registrador_4bits port map(
        clock=>clock,
        clear=>limpaR,
        enable=>registraR,
        D=>botoes,
        Q=>s_jogada);
    db_jogada<=s_jogada;
    or_JGD<=botoes(0) or botoes(1) or botoes(2) or botoes(3);
    JGD: edge_detector port map(
        clock=>clock,
        reset=>zeraE,
        sinal=>or_JGD,
        pulso=>jogada_feita
    );
    db_tem_jogada<=or_JGD;
end architecture;

```

Diagrama:

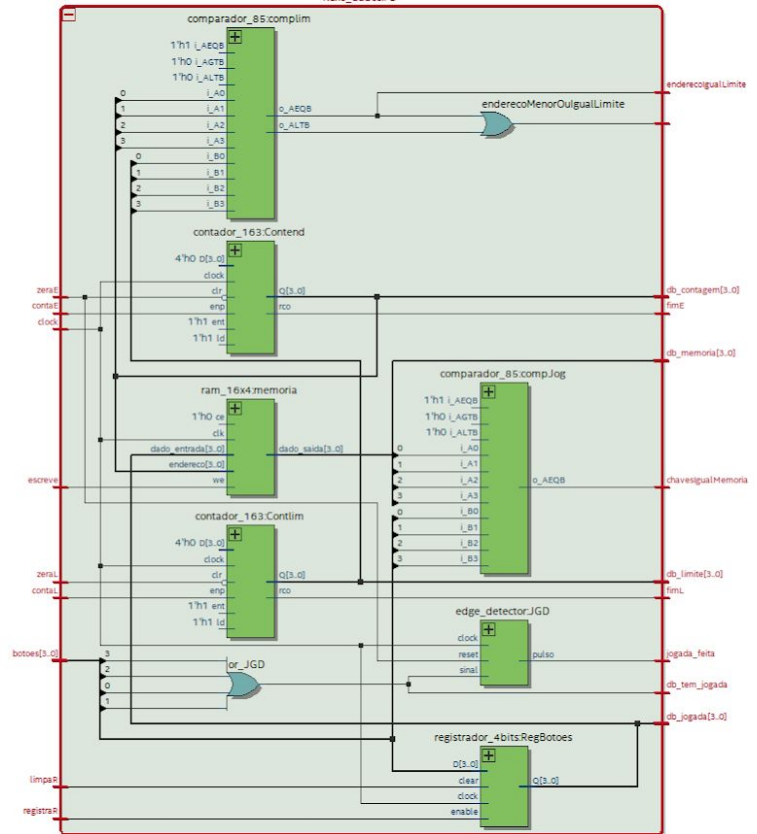

E por fim o circuito segue:

```
library ieee;
use ieee.std_logic_1164.all;
entity circuito_exp6 is
    port (
        clock : in std_logic;
        reset : in std_logic;
        iniciar : in std_logic;
        botoes : in std_logic_vector (3 downto 0);
        acertou : out std_logic;
        errou : out std_logic;
        pronto : out std_logic;
        leds: out std_logic_vector (3 downto 0);
        db_limite : out std_logic_vector (6 downto 0);
        db_igual : out std_logic;
        db_contagem : out std_logic_vector (6 downto 0);
        db_memoria : out std_logic_vector (6 downto 0);
        db_estado : out std_logic_vector (6 downto 0);
        db_jogada : out std_logic_vector (6 downto 0);
        db_clock : out std_logic;
```

```

        db_tem_jogada : out std_logic

    );
end entity;

architecture estrutural of circuito_exp6 is
    component fluxo_dados is
        port(
            clock : in std_logic;
            zeraE : in std_logic;
            limpaR: in std_logic;
            registraR: in std_logic;
            zeraL: in std_logic;
            contaL: in std_logic;
            contaE : in std_logic;
            escreve: in std_logic;
            botoes : in std_logic_vector (3 downto 0);
            fimE: out std_logic;
            fimL: out std_logic;
            db_tem_jogada: out std_logic;
            db_contagem : out std_logic_vector (3 downto 0);
            db_memoria: out std_logic_vector(3 downto 0);
            db_limite: out std_logic_vector (3 downto 0);
            jogada_feita: out std_logic;
            db_jogada: out std_logic_vector (3 downto 0);
            chavesIgualMemoria: out std_logic;
            enderecoMenorOuIgualLimite: out std_logic;
            enderecoIgualLimite: out std_logic
        );
    end component;

    component unidade_controle is
        port(
            clock:      in  std_logic;
            reset:      in  std_logic;
            iniciar:    in  std_logic;
            fimC:       in  std_logic;
            fimL:       in  std_logic;
            jogada:     in  std_logic;
            enderecoIgualLimite: in std_logic;

```

```

zera:      out std_logic;
conta_end: out std_logic;
conta_lim: out std_logic;
zera_lim:  out std_logic;
pronto:    out std_logic;
db_estado: out std_logic_vector(3 downto 0);
acertou:   out std_logic;
errou:     out std_logic;
registra:  out std_logic;
igual:     in std_logic
    );
end component;

component hexa7seg is
    port (
        hexa : in  std_logic_vector(3 downto 0);
        sseg : out std_logic_vector(6 downto 0)
    );
end component;

    signal      conta4, memo4, estad4, joga4, lim4, botoes_led:
std_logic_vector (3 downto 0);
    signal conta, fim, zeraE, registra, clk, jogada, igual_i: std_logic;
                                                    signal
zeraL, contaL, contaE, fimE, fimL, jogada_feita, chavesIgualMemoria, endere
coIgualLimite: std_logic;
begin
    leds(0) <= botoes(0);
    leds(1) <= botoes(1);
    leds(2) <= botoes(2);
    leds(3) <= botoes(3);
    clk <= clock;
    FD: fluxo_dados port map(
        clock => clk,
        zeraE => zeraE,
        limpaR => zeraE,
        registraR => registra,
        zeraL => zeraL,
        contaL => contaL,
        contaE => contaE,

```

```

escreve=>'1',
botoes =>botoes,
fimE=>fimE,
fimL=>fimL,
db_tem_jogada=>db_tem_jogada,
db_contagem =>conta4,
db_memoria=>memo4,
db_limite=>lim4,
jogada_feita=>jogada_feita,
db_jogada=>joga4,
chavesIgualMemoria=>chavesIgualMemoria,
enderecoIgualLimite=>enderecoIgualLimite
);
db_igual<=igual_i;
UC: unidade_controle port map(
    clock=>clock,
    reset=>reset,
    iniciar=>iniciar,
    fimC=>fimE,
    fimL=>fimL,
    jogada=>jogada_feita,
    enderecoIgualLimite=>enderecoIgualLimite,
    zera=>zeraE,
    conta_end=>contaE,
    conta_lim=>contaL,
    zera_lim=>zeraL,
    pronto=>pronto,
    db_estado=>estad4,
    acertou=>acertou,
    errou=>errou,
    registra=>registra,
    igual=>chavesIgualMemoria
);
db_clock<=clk;
HEX1: hexa7seg port map(
    hexa =>conta4,
    sseg =>db_contagem
);

HEX2: hexa7seg port map(

```

```

        hexa =>memo4,
        sseg =>db_memoria
    );

    HEX3: hexa7seg port map(
        hexa =>estad4,
        sseg =>db_estado
    );

    HEX4: hexa7seg port map(
        hexa=>joga4,
        sseg=> db_jogada
    );
    HEX5: hexa7seg port map(
        hexa=>lim4,
        sseg=> db_limite
    );
end architecture;

```

2.3) Plano de testes


Cenário #1 – Acerto de todas as jogadas				
#	Operação	Sinais de Entrada	Resultado Esperado	Resultado Observado
c.i.	Condições Iniciais			
1	Iniciar ciclo	iniciar = 1		
2	Acertar jogada	botoes = 0001	igual = 1	
3	Acertar jogada	botoes = 0001, botoes = 0010	igual = 1	
4	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100	igual = 1	
5	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000	igual = 1	
6	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000, botoes = 0100	igual = 1	

7	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000, botoes = 0100, botoes = 0010	igual = 1	
8	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000, botoes = 0100, botoes = 0010, botoes = 0001	igual = 1	
9	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000, botoes = 0100, botoes = 0010, botoes = 0001, botoes = 0001	igual = 1	
10	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000, botoes = 0100, botoes = 0010, botoes = 0001, botoes = 0001, botoes = 0010	igual = 1	
11	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000, botoes = 0100, botoes = 0010, botoes = 0001, botoes = 0001, botoes = 0010, botoes = 0010	igual = 1	
12	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000, botoes = 0100, botoes = 0010, botoes = 0001, botoes = 0001, botoes = 0010, botoes = 0010, botoes = 0100	igual = 1	
13	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000, botoes = 0100, botoes = 0010, botoes = 0001, botoes = 0001, botoes = 0010, botoes = 0010, botoes = 0100, botoes = 0100	igual = 1	
14	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000, botoes = 0100, botoes = 0010, botoes = 0001, botoes = 0001, botoes = 0010, botoes = 0010, botoes = 0100, botoes = 0100, botoes = 1000	igual = 1	
15	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000, botoes = 0100, botoes = 0010, botoes = 0001, botoes = 0001, botoes = 0010, botoes = 0010, botoes = 0100, botoes = 0100, botoes = 1000, botoes = 1000	igual = 1	
16	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000,	igual = 1	

		botoes = 0100, botoes = 0010, botoes = 0001, botoes = 0001, botoes = 0010, botoes = 0010, botoes = 0100, botoes = 0100, botoes = 1000, botoes = 1000, botoes = 0001		
17	Acertar jogada	botoes = 0001, botoes = 0010, botoes = 0100, botoes = 1000, botoes = 0100, botoes = 0010, botoes = 0001, botoes = 0001, botoes = 0010, botoes = 0010, botoes = 0100, botoes = 0100, botoes = 1000, botoes = 1000, botoes = 0001, botoes = 0100	igual = 1, pronto = 1, acertou = 1	

Cenário #2 – Erro na 4ª jogada				
#	Operação	Sinais de Entrada	Resultado Esperado	Resultado Observado
c.i.	Condições Iniciais			
1	Iniciar Ciclo	iniciar = 1		
2	Acertar jogadas	botoes = 0001	igual = 1	
3		botoes = 0001, botoes = 0010	igual = 1	
4		botoes = 0001, botoes = 0010, botoes = 0100	igual = 1	
5	Errar jogada	botoes = 0010	pronto = 1, errou = 1	

2.4) Simulação do circuito

 

2.5) Designação de pinos

Sinal	Pino na Placa DE0-CV	Pino no FPGA	Analog Discovery
CLOCK	GPIO_0_D13	PIN_T22	StaticIO – LED – DIO0 Patterns – Clock – 1kHz
RESET	GPIO_0_D15	PIN_N19	StaticIO – Button 0/1 – DIO1
INICIAR	GPIO_0_D17	PIN_P19	StaticIO – Button 0/1 – DIO2
BOTOES(0)	GPIO_0_D19	PIN_P17	StaticIO – Button 0/1 – DIO3
BOTOES(1)	GPIO_0_D21	PIN_M18	StaticIO – Button 0/1 – DIO4
BOTOES(2)	GPIO_0_D23	PIN_L17	StaticIO – Button 0/1 – DIO5
BOTOES(3)	GPIO_0_D25	PIN_K17	StaticIO – Button 0/1 – DIO6
LEDS(0)	Led LEDR0	PIN_AA2	-
LEDS(1)	Led LEDR1	PIN_AA1	-
LEDS(2)	Led LEDR2	PIN_W2	-
LEDS(3)	Led LEDR3	PIN_Y3	-

PERDEU	Led LEDR7	PIN_U1	-
GANHOU	Led LEDR8	PIN_L2	-
PRONTO	Led LEDR9	PIN_L1	-
db_chavesIgualMemoria	Led LEDR4	PIN_N2	-
db_clock	Led LEDR5	PIN_N1	-
db_tem_jogada	Led LEDR6	PIN_U2	-
db_contagem	Display HEX0	[0] PIN_U21 [1] PIN_V21 [2] PIN_W22 [3] PIN_W21 [4] PIN_Y22 [5] PIN_Y21 [6] PIN_AA22	-
db_memoria	Display HEX1	[0] PIN_AA20 [1] PIN_AB20 [2] PIN_AA19 [3] PIN_AA18 [4] PIN_AB18 [5] PIN_AA17 [6] PIN_U22	-
db_jogada	Display HEX2	[0] PIN_Y19 [1] PIN_AB17 [2] PIN_AA10 [3] PIN_Y14 [4] PIN_V14 [5] PIN_AB22 [6] PIN_AB21	-
db_limite	Display HEX3	[0] PIN_Y16 [1] PIN_W16 [2] PIN_Y17 [3] PIN_V16 [4] PIN_U17 [5] PIN_V18 [6] PIN_V19	-
db_estado	Display HEX5	[0] PIN_N9 [1] PIN_M8 [2] PIN_T14 [3] PIN_P14 [4] PIN_C1 [5] PIN_C2 [6] PIN_W19	-